



Government Polytechnic, Kishanganj

Assignment-01

Course: Diploma

Subject Name: E.M&T

Branch- E.E

Semester: III

Q.1 The function of oil in a transformer is

- (a) to provide insulation and cooling
- (b) to provide protection against lightning
- (c) to provide protection against short-circuit
- (d) to provide lubrication

Q.2 Explain principle of operation of two winding Transformer, also draw the equivalent circuit diagram of a two Winding Transformer.

Q.3 Draw the connection diagram of Y/d/30° or Y/d/11 Transformer.

Q.4 The efficiency of a 100 kVA transformer is 0.98 at full as well as at half load. For this transformer at full load the copper loss

- (a) is less than core loss
- (b) is equal to core loss
- (c) is more than core loss
- (d) none of the above

Q.5 A 400V/100 V, 10 KVA two winding transformer is reconnected as an auto transformer across a suitable voltage source. The maximum rating of such an arrangement could be

- (a) 50 kVA
- (b) 15 kVA
- (c) 12.5 kVA
- (d) 8.75 kVA

Q.6 Write the advantage and disadvantage of Auto-transformer.

Q.7 Derive the condition for maximum efficiency in case of single-phase transformer and also find output KVA corresponding to maximum efficiency

Q.8 A 10 kVA, 400/200 V, single-phase transformer with a percentage resistance of 3% and percentage reactance of 6% is supplying a current of 50 A to a resistive load. The value of load voltage is

- (a) 194 V
- (b) 390 V
- (c) 192 V
- (d) 196 V

Q.9 Draw the equivalent circuit of O.C and S.C Test of single phase transformer and thus determine the equivalent parameters.